

## PSL-3604 – Hardware Upgrade

Boards rev. 1

1. There is an error in the schematic of the front panel – pins 11 and 12 of register U4 are mixed up. It is corrected by jumpers, the necessary vias are located next to it (Fig. 1). Pin tracks 11 and 12 are trimmed before jumpers are installed.

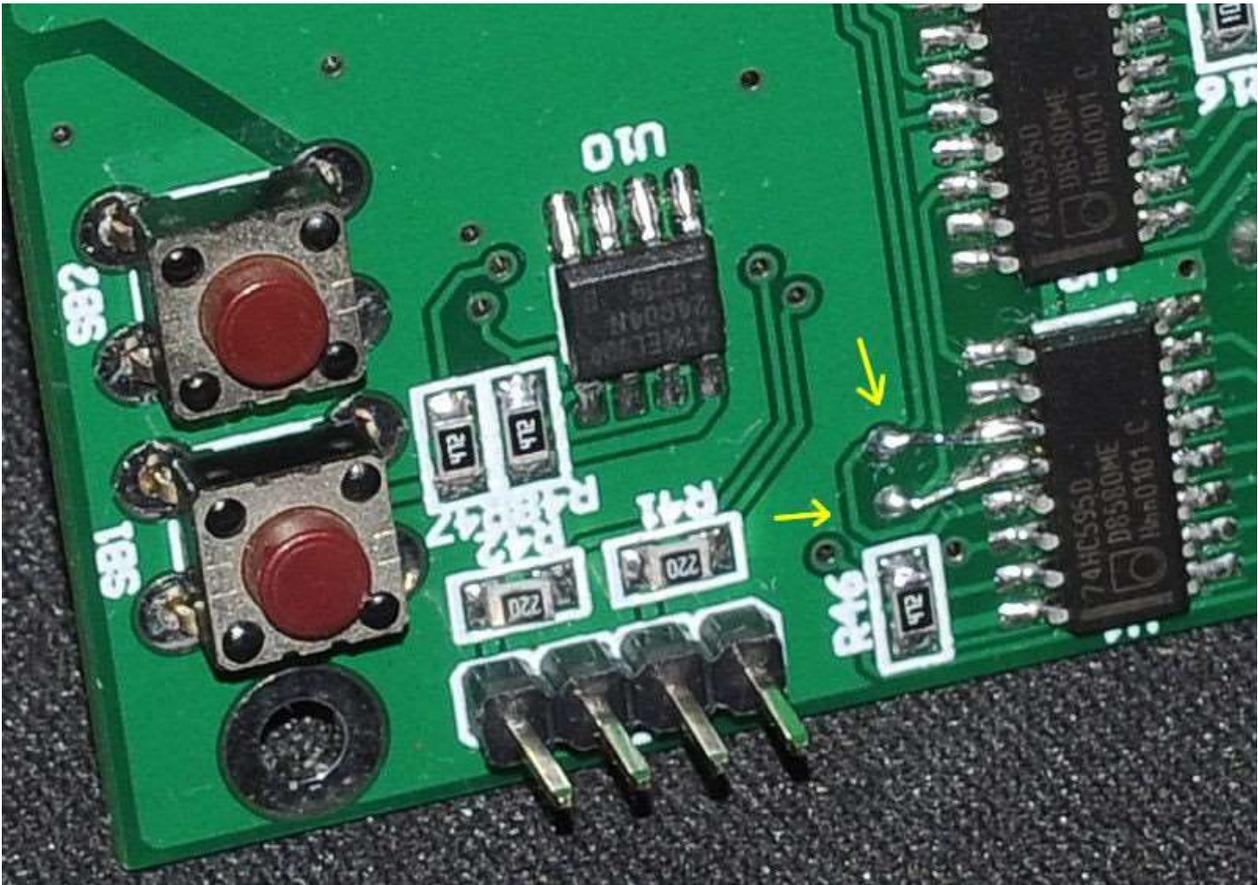


Fig. 1.

2. The processor has been replaced with STM32F100C8T6BB (Fig. 2).
3. There was an ADC error of several units. It is corrected by replacing the C2 and C4 capacities at the input of the ADC with 220 pF (Fig. 2).  
Explanation here: read [STM32 ISSUE](#)

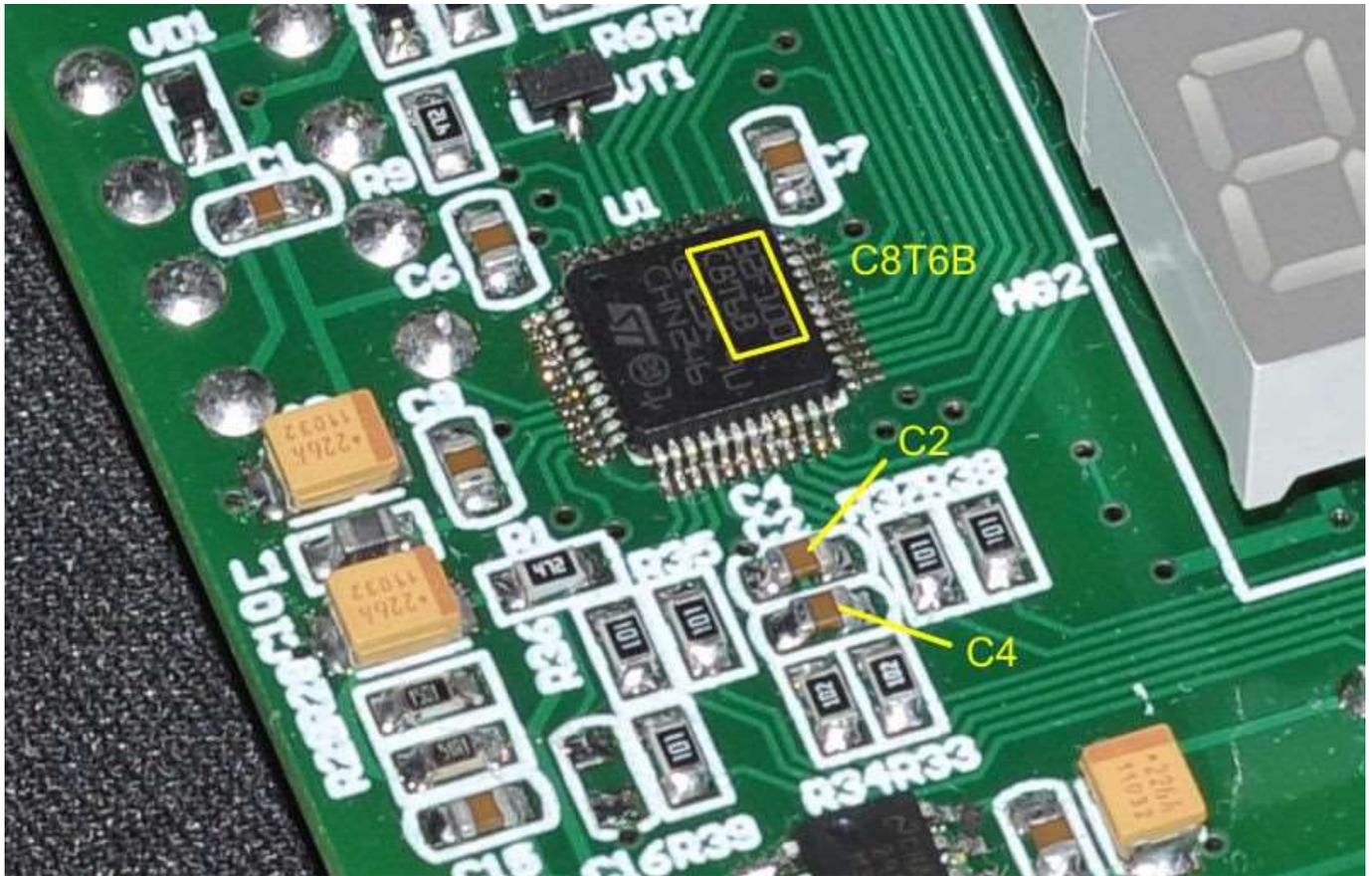


Fig. 2.

- The voltage across the C20 capacitor is about 48V, which is close to the maximum (50V). Replace the C20 capacitor with 2200  $\mu\text{F}$  x 63 V (Fig. 3). Such a replacement is only required if the transformer used provides such a high voltage. For lower voltage versions of the PSU, replacement is not required.
- The voltage at the input of the regulator is -5 V too high (about 20 V). Capacitors C1 and C3 need to be replaced with 47  $\mu\text{F}$  x 100 V (Fig. 3). In this case, the voltage is reduced to about 13 V, which is normal.



Fig. 3.

6. Remove components VD20, R78 (number 1 in Figure 4). It is enough to remove one of the components, I did not remove the diode. In principle, they are not very disturbing, but there is not much benefit either. Components were introduced to reduce the downward surge that was observed when the voltage was abruptly reduced at some load capacitances. But the emission is very small (about 100 mV), there is no point in fighting.
7. Replace the R89 on the power board with 5.1 k $\Omega$  to correctly detect the status of the incoming output current (number 2 in Figure 4). Here there were disagreements with the simulator, he is too optimistic about the maximum range of voltage at the output of the op amp.
8. To detect the Unregulated status, the input of the U10 comparator (LM358) must be disconnected from the output of the current error amplifier by removing R80 (number 3 in Fig. 4). A hole is drilled on the R80 pad, through which the jumper connecting pin 2 U10 to the GNDA polygon is soldered. Modification is not mandatory, with it the PSU will signal a situation when it is unable to maintain the output voltage (for example, due to a network drawdown).

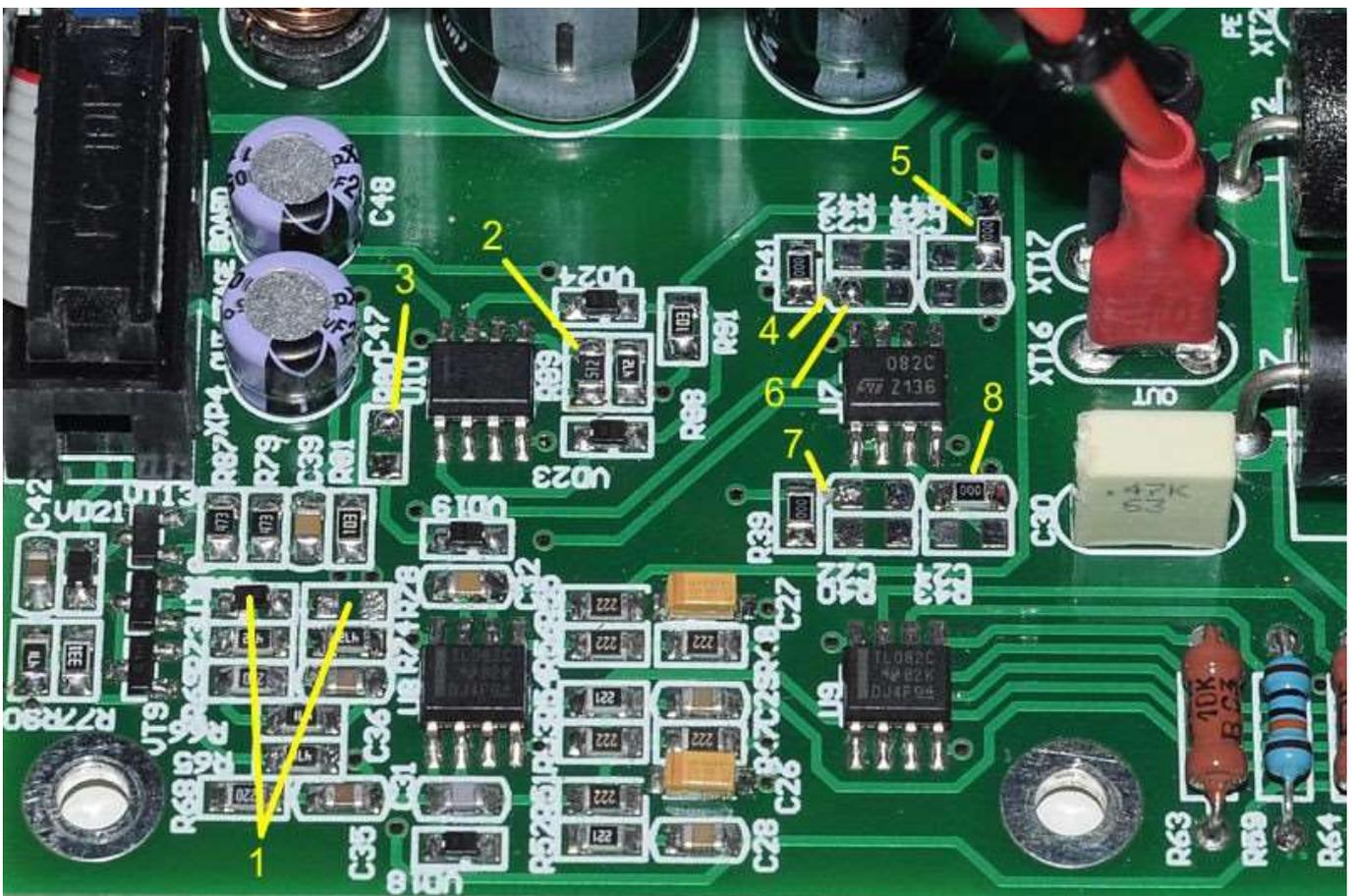


Fig. 4.

9. The COM voltage divider on the front panel board has too high an output impedance, so there is an error in measuring current and voltage. To fix the error, you need to add a repeater to the output of the op amp. To do this, you can use the DAC filter op amp. In this case, you don't need an active filter,



11. When there is a transition between the two levels of current stabilization, a surge is observed. To eliminate it, you need to add a chain of R98 10 k $\Omega$  and C51 1 nF. First, an R98 resistor of size 1206 (shown in red in Fig. 6) is mounted on the board above the C32, C51 of size 0805 is soldered to it (shown in blue in Fig. 6), which is soldered to the R78 pad with the second pin.

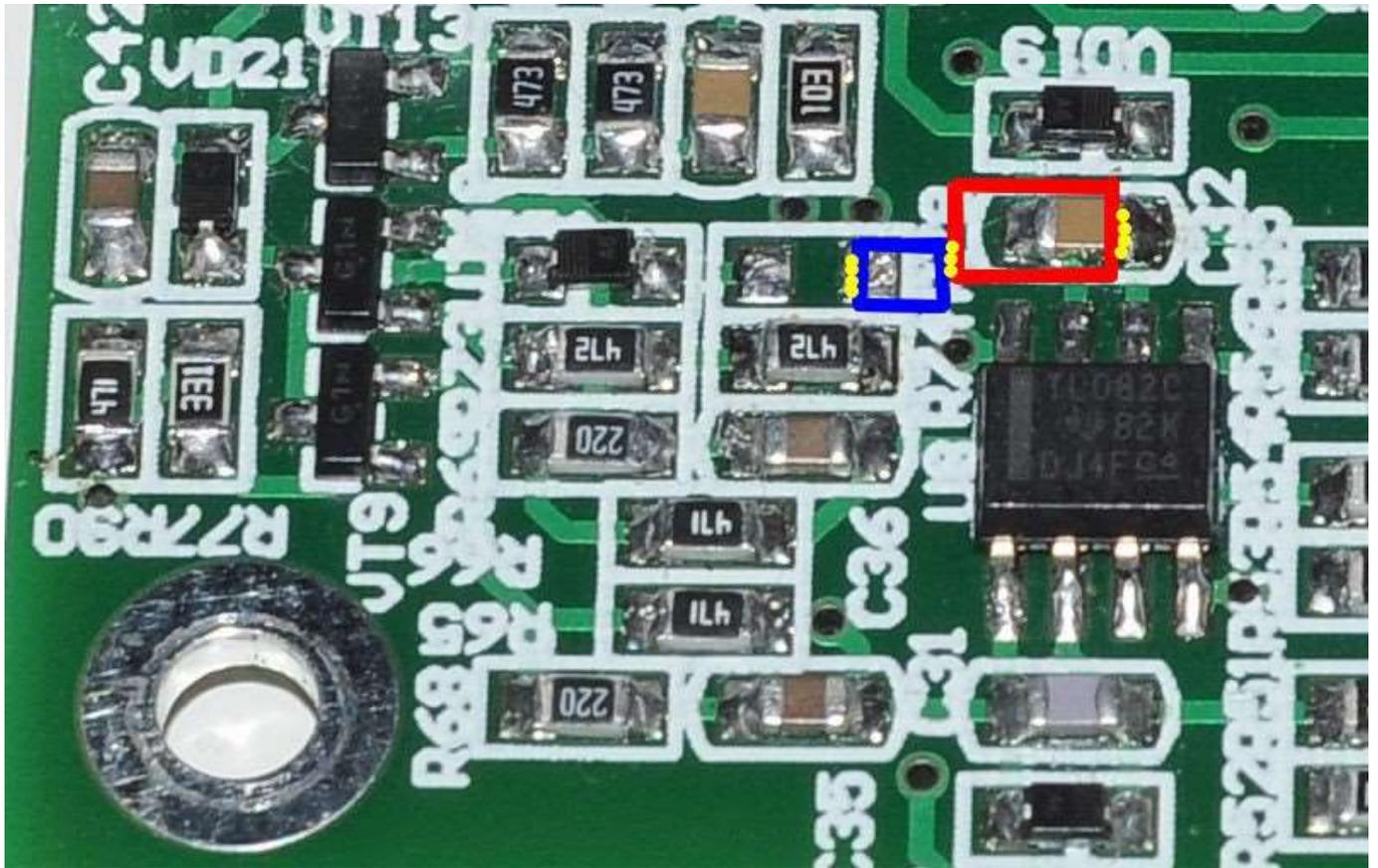


Fig. 6.





14. In parallel with the resistors R25 – R28 on the output stage board, I installed another resistor of the same kind in parallel (Fig. 9). As a result, the scattering power was reduced to an acceptable value.

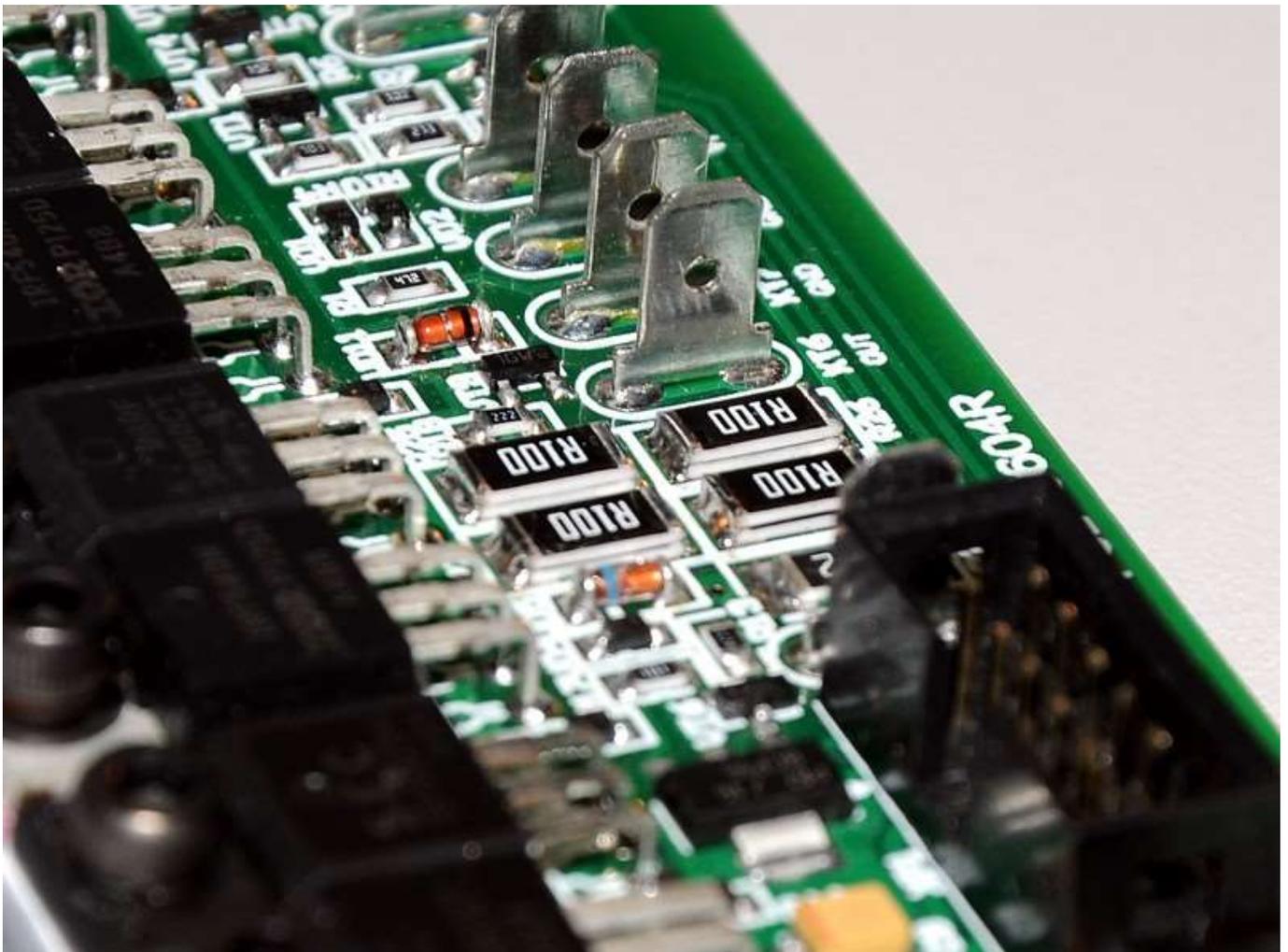


Fig. 9.

15. **Modification is not necessary** - to reduce the interference voltage on the COM signal relative to GND, connect the XT17 terminal (GND) on the main board to the power ground polygon (minus the C18 capacitor) (Fig. 10).



Fig. 10.

16. **Modification is not necessary** - when the power is turned off, all sorts of unnecessary values flash on the display, the sound emitter beeps. To fix the problem, you need to add a power detector circuit (see Figure 11). The circuit can be assembled by any method of mounting on the main board (Fig. 12). The output of this circuit is wound onto the pin, then connected to the pin on the front panel board with a wire (Fig. 14). It is pressed into a hole with a diameter of 0.7 mm drilled at the point marked in Fig. 13. The pin is connected by a jumper to pin 33 (PA12) of the controller (Fig. 15).

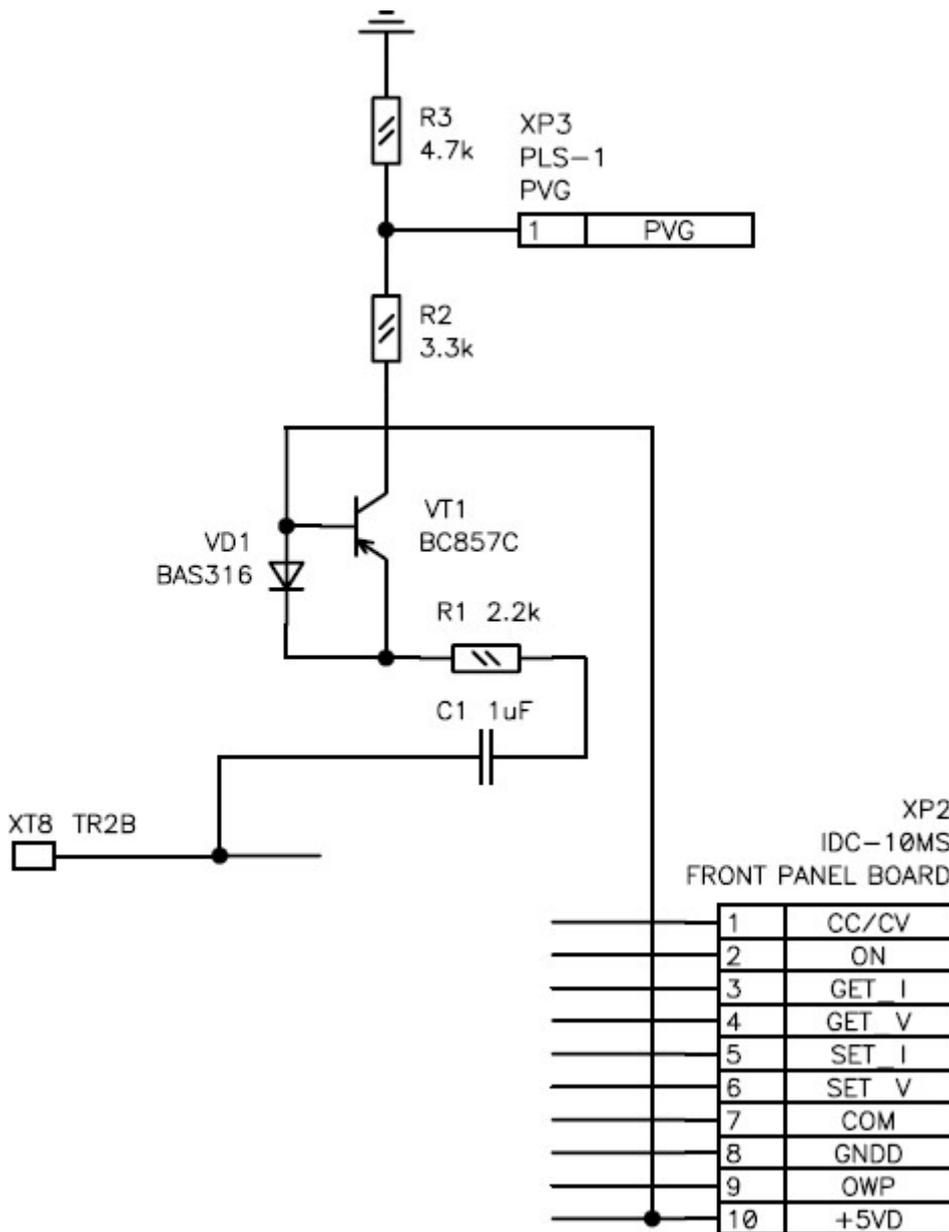


Fig. 11.

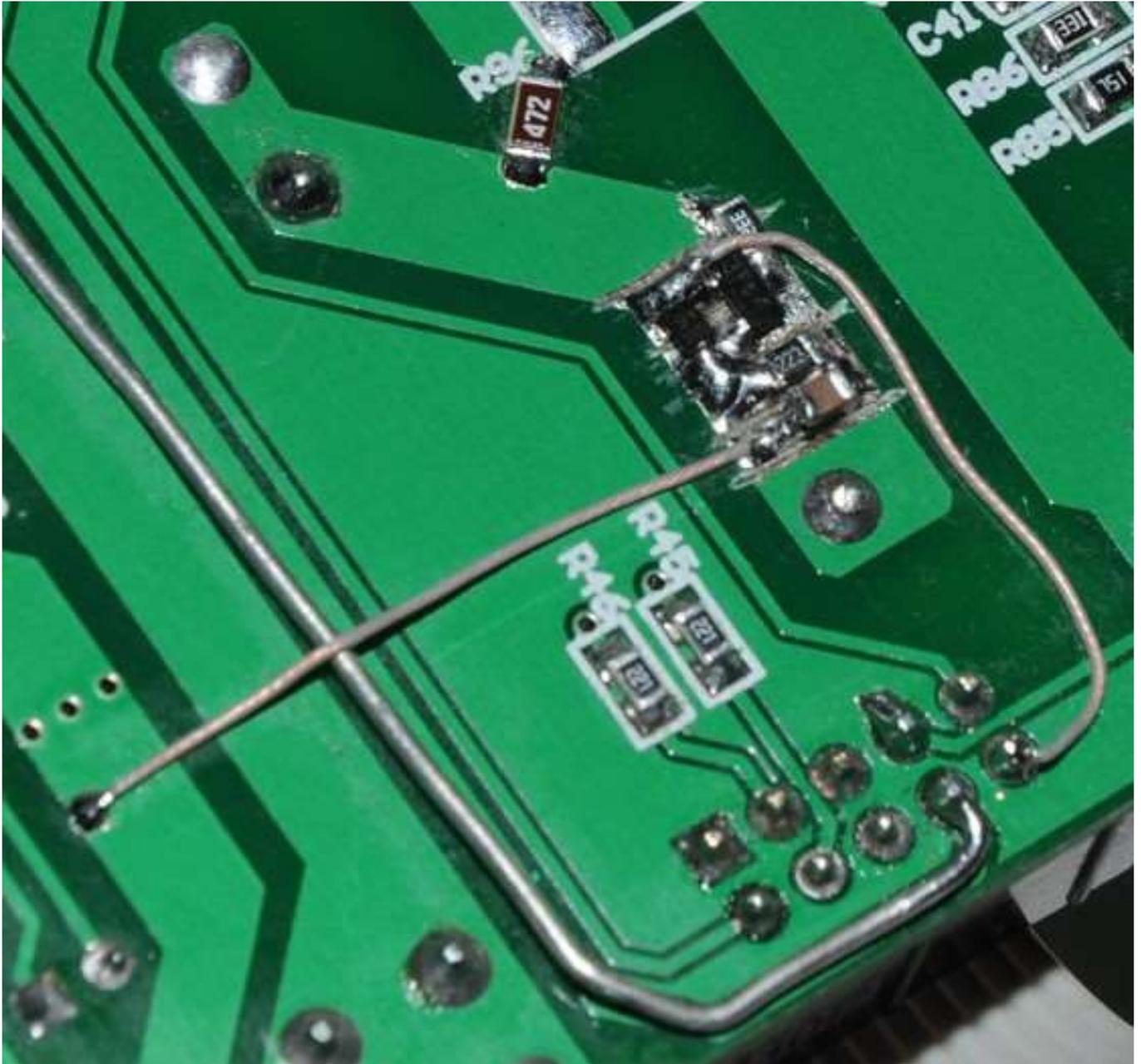


Fig. 12.

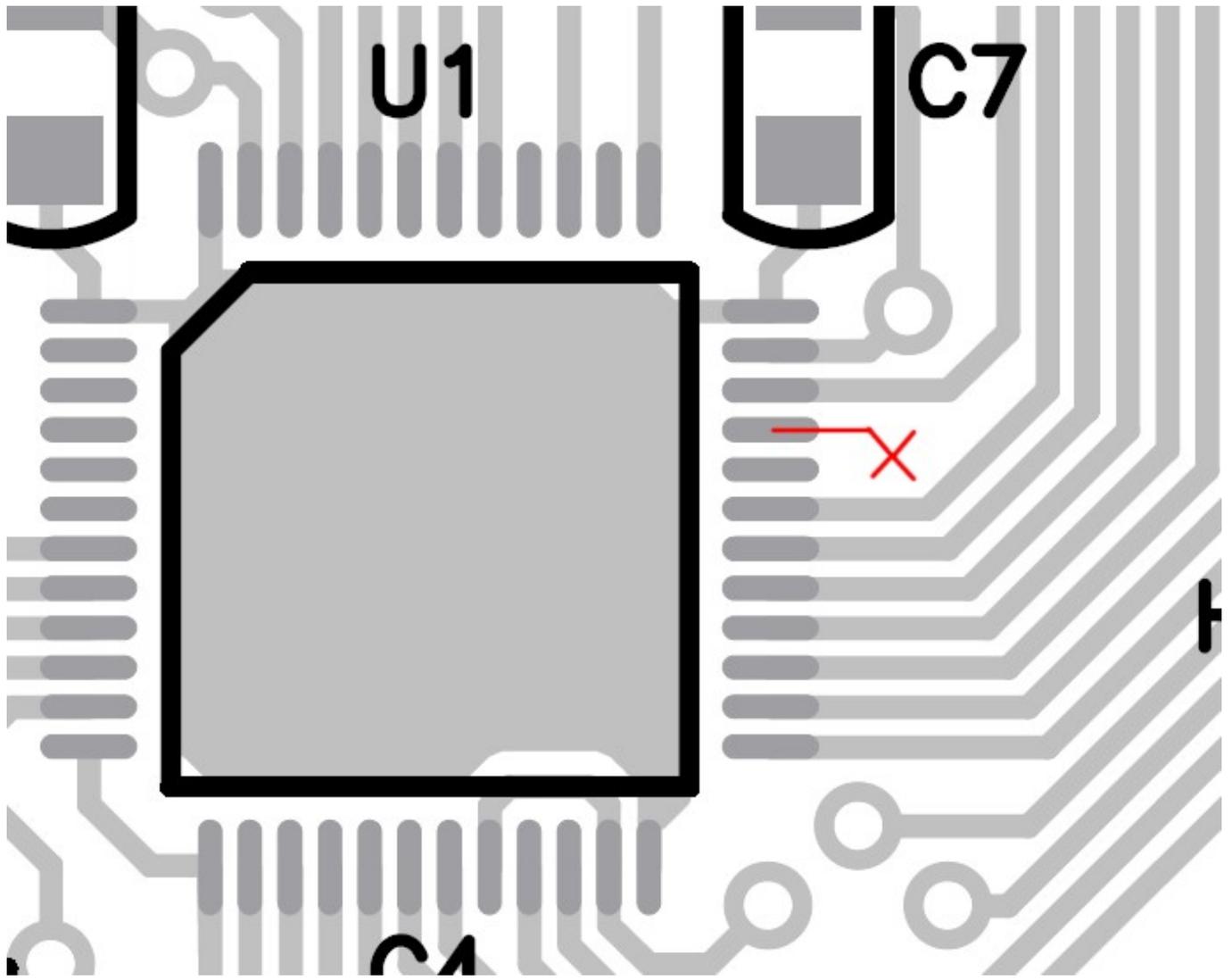


Fig. 13.

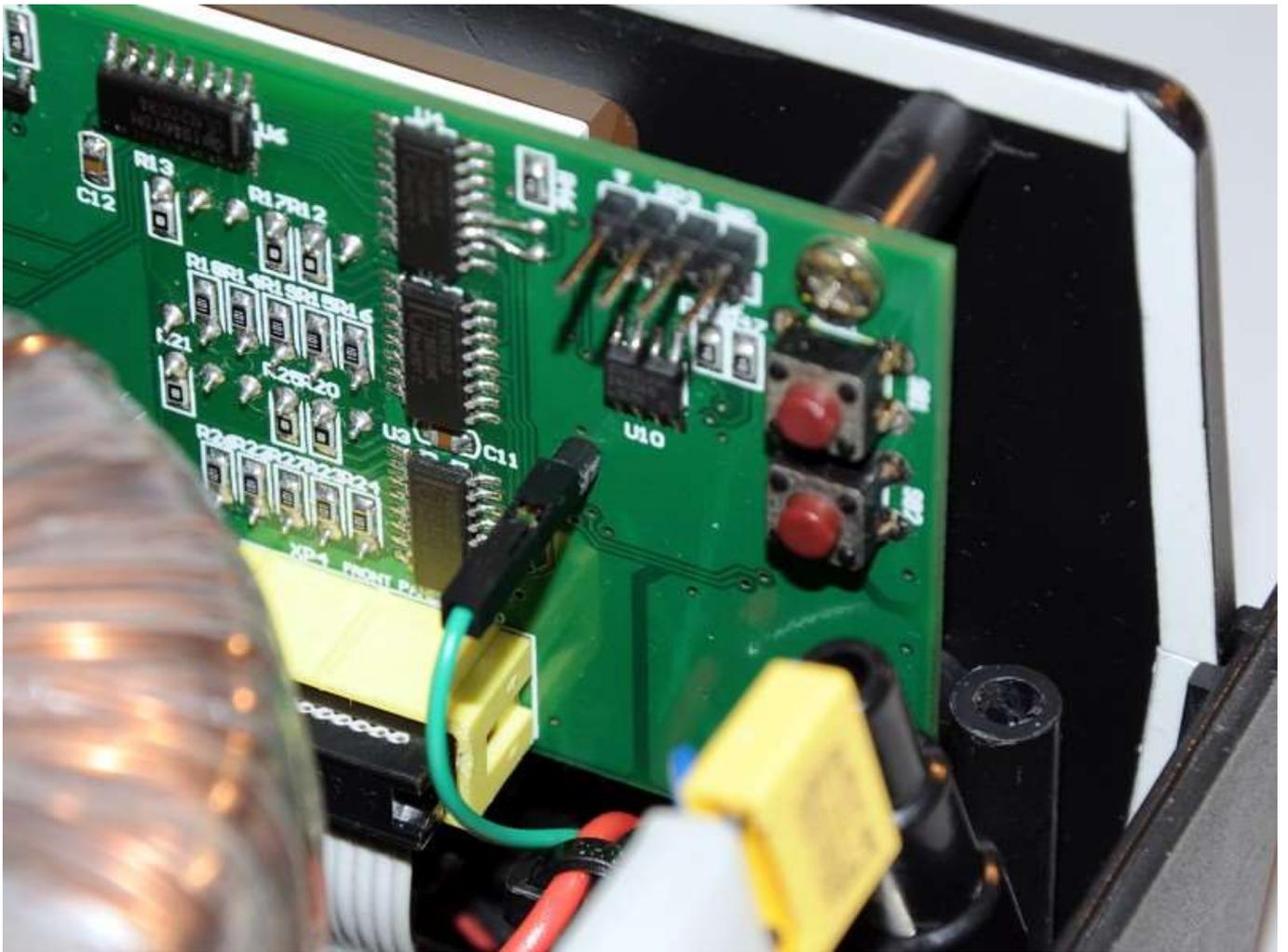


Fig. 14.

